

Objectives

This lab is organized as follows:

1. An introduction
2. Experiments to be conducted
3. Lab Report Requirements

As studied in the lectures, RISC-V can be implemented such that each instruction is executed in a single clock cycle as shown in Figure 1. As in the lectures we will focus on supporting the following RV32I ISA subset:

- Memory reference: LW (I-Format), SW (S-Format)
- Arithmetic/logical: ADD, SUB, AND, OR (R-Format)
- Control transfer: BEQ (SB-Format)

The goal of this lab is to model and simulate some of the non-memory components necessary for this implementation.

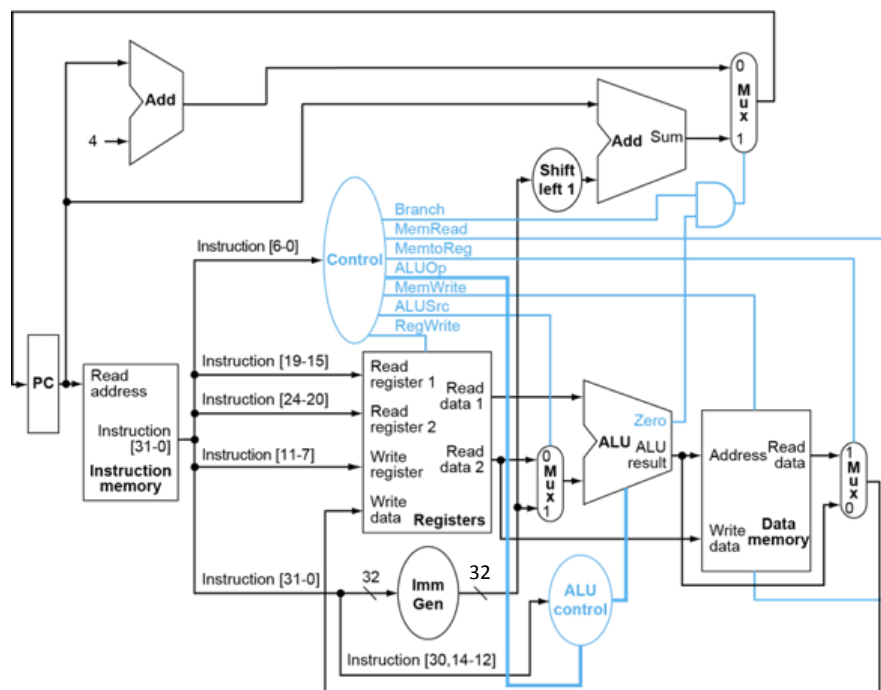


Figure 1: RISC-V Single Cycle Datapath

Table 1 shows the instruction encoding for the RV32I instructions highlighting the instructions we will implement in this lab. Note that:

- For our subset, the 7-bit opcode field is enough to decode the instruction except for R-Format instructions (ADD, SUB, AND, OR) which all have the same value (0110011) for that field. For R-Format instructions, the actual operation is determined by the funct3 and funct7 fields (only bit 30 from the funct7 field is needed).
- The least significant 2 bits of the 7-bit opcode field are always 11 and as such can be excluded from any decoding circuit inputs.

Table 1: RV32I instructions encoding

imm[31:12]				rd	0110111	LUI	
imm[31:12]				rd	0010111	AUIPC	
imm[20:10:11:19:12]				rd	1101111	JAL	
imm[11:0]			rs1	000	rd	1100111	JALR
imm[12:10:5]	rs2	rs1	000	imm[4:1:11]	1100011	BEQ	
imm[12:10:5]	rs2	rs1	001	imm[4:1:11]	1100011	BNE	
imm[12:10:5]	rs2	rs1	100	imm[4:1:11]	1100011	BLT	
imm[12:10:5]	rs2	rs1	101	imm[4:1:11]	1100011	BGE	
imm[12:10:5]	rs2	rs1	110	imm[4:1:11]	1100011	BLTU	
imm[12:10:5]	rs2	rs1	111	imm[4:1:11]	1100011	BGEU	
imm[11:0]			rs1	000	rd	0000011	LB
imm[11:0]			rs1	001	rd	0000011	LH
imm[11:0]			rs1	010	rd	0000011	LW
imm[11:0]			rs1	100	rd	0000011	LBU
imm[11:0]			rs1	101	rd	0000011	LHU
imm[11:5]	rs2	rs1	000	imm[4:0]	0100011	SB	
imm[11:5]	rs2	rs1	001	imm[4:0]	0100011	SH	
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	SW	
imm[11:0]			rs1	000	rd	0010011	ADDI
imm[11:0]			rs1	010	rd	0010011	SLTI
imm[11:0]			rs1	011	rd	0010011	SLTIU
imm[11:0]			rs1	100	rd	0010011	XORI
imm[11:0]			rs1	110	rd	0010011	ORI
imm[11:0]			rs1	111	rd	0010011	ANDI
0000000	shamt	rs1	001	rd	0010011	SLLI	
0000000	shamt	rs1	101	rd	0010011	SRLI	
0100000	shamt	rs1	101	rd	0010011	SRAI	
0000000	rs2	rs1	000	rd	0110011	ADD	
0100000	rs2	rs1	000	rd	0110011	SUB	
0000000	rs2	rs1	001	rd	0110011	SEI	
0000000	rs2	rs1	010	rd	0110011	SLT	
0000000	rs2	rs1	011	rd	0110011	SLTU	
0000000	rs2	rs1	100	rd	0110011	XOR	
0000000	rs2	rs1	101	rd	0110011	SRL	
0100000	rs2	rs1	101	rd	0110011	SRA	
0000000	rs2	rs1	110	rd	0110011	OR	
0000000	rs2	rs1	111	rd	0110011	AND	

In this lab we are going to model and test the following components:

1. A 32-bit register with reset and load control (to be used for PC and to construct the register file)
2. A 32-bit 2x1 multiplexer
3. A 32-bit shift left 1 module
4. The immediate generator & sign extender module

Note: Students should be working in pairs to implement the following experiments

Experiments

Experiment 1: A 32-bit register with reset and load control

Create and simulate a module representing a 32-bit register with load control like the one shown in Figure 2.

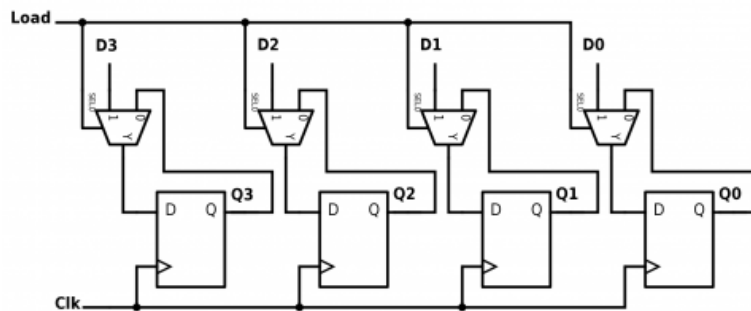


Figure 2: Register with load control

- a) Design a D flip flop module with asynchronous reset input. You can define the flip flop module with reset (not shown in the above diagram) as follows:

```
module DFlipFlop
  (input clk, input rst, input D, output reg Q);

  always @ (posedge clk or posedge rst) begin    // Asynchronous Reset
    if (rst)
      Q <= 1'b0;
    else
      Q <= D;
    end
endmodule
```

- b) Design a 2x1 multiplexer (implemented as shown in Figure 3).

 


Figure 3: 2x1 Multiplexer

- c) Design a 32-bit register module using the modules of part a. To avoid repeating your code 32 times, use a `generate` loop.
- d) Develop a testbench to test the 32-bit register.

Remember: the code below creates a clock signal in a testbench with a period of 20 ns.

```
initial begin
  clk = 0;
  forever #10 clk=~clk;
end
```

Experiment 2: A 32-bit 2x1 multiplexer

Create and simulate a module representing a 32-bit 2x1 multiplexer. The module's structure should be an array of 2x1 multiplexers. Again use a `generate` loop to do it.

Experiment 3: A 32-bit shift left 1 module

Create and simulate a module representing a 32-bit shift left 1 module. Shifting should be done by rewiring inputs. (**Don't use shift operator**)

Experiment 4: The immediate generator & sign extender module

This module has to take into consideration different instruction formats to be able to generate the appropriate immediate constant. Figure 4 shows the instruction formats for all supported instructions with immediate operands. LW uses the I-Format, SW uses the S-Format, while BEQ uses the SB-Format. So an immediate generator should receive the entire instruction to decide which 12 bits to use (based on the opcode and funct3 bits if needed).

More specifically, the immediate generator must choose between

- sign extending a 12-bit field in instruction bits 31:20 for LW
- a concatenation of bits 31:25 and 11:7 for SW
- a concatenation of bits 31, 7, 30:25, and 11:8 for BEQ

It turns out that opcode bit 6 is equal to 0 for LW and SW and equal to 1 for BEQ. Also opcode bit 5 is 0 for LW and 1 for SW. So the immediate generator can rely on these 2 bits to decide how to form the 12 bits to extend.

 


Figure 4 Instruction Formats for Supported Instructions with Immediate Operands

Here is the immediate generator module skeleton that you should complete and simulate.

```
module ImmGen (output [31:0] gen_out, input [31:0] inst);
    ...
    ...
    ...
Endmodule
```

Below are some test cases to try out:

inst	gen_out	Instruction info
32'h4D62A303	1238 (binary 010011010110)	LW 010011010110 00101 010 00110 0000011
32'hDCA7AF23	-546 (binary 1101110 11110)	SW 1101110 01010 01111 010 11110 0100011
32'h18E18F63	207 (binary 0 0 001100 1111)	BEQ 0001100 01110 00011 000 11110 1100011

Deliverables

General Report Submission Notes:

- Each student is required to submit an individual report.
- The submission should be composed of **two files only**:
 - YourID_Report.pdf/doc:
A single pdf/word file having the solution of the lab report questions in correct sequence.
 - YourID_labwork.zip/rar/...:
A zipped folder containing your codes for all the lab experiments organized in sequence.
- Submission deadline**: half an hour before the start of next week's session.
- Submission method**: On Blackboard

Lab Report [10 pts]

- [0 pts] Your name and student ID.
- [2 pts] A technical summary of experiments conducted in the lab (Steps, Results, components (a screen shot with Schematic design might help), code functionality, etc...).
- [2 pts] Verilog code for all modules of each experiment, and Verilog code for the testbench module of each experiment's top-level module.
- [2 pts] Snapshot of simulation output corresponding to the submitted testbench with a **brief interpretation** of the snapshot.
- [2 pts] Consider an n-bit register with *reset*, *load* and *shift* control inputs. Whenever *load* equals 1 an n-bit input is loaded to the register. Whenever *shift* equals 1 the register data should get shifted 1 bit to the right. If both *shift* and *load* equal 1, *load* should have a higher priority than *shift* and a load operation is carried on.
Develop the Verilog code for this register. The module should be parametrized with a default value of 32 for n.
- [1 pts] Develop a schematic showing the internal design the previous module (Hint: look for it in Vivado).
- [1 pts] Sketch a schematic of a 16-bit ALU circuit that allows up to 8 different arithmetic and logic operations.